

NARULAINSTITUTEOFTECHNOLOGY

81, Nilgunj Road, AgarparaKolkata-700109,WestBengal

<u>DepartmentofElectricalEngineering</u>.

Projectof:BasicElectronicsEngineering.

Papercode:PR291

Topic:Zenerdiodeasvoltageandlineregulator.

Groupmembersname	
Ayushi Gupta	
Biswadip Kundu	
DaminiSaha	
AsmitaMalakar	
Jayanta Saha	
Madhurima Das	
HiravraKoley	

Say

Alarina marifula of Tachnology

Narrina marifula of Tachnology

Narrina marifula of Tachnology

Narrina marifula of Tachnology

Teacher's Signature

• <u>Title:</u> Zener diode characteristics as line and load regulator.

• Introduction to the topic:

A voltage regulator is an electronic circuit that provides a stable DC voltage independent of the load current, temperature and AC line voltage variations. A zener diode of break down Vz is reverse connected to an input voltage source V_1 across a load resistance R_L and a series resistor R_S . The voltage across the zener will remain steady at its break down voltage V_Z for all the values of zener current I_Z as long as the current remains in the breakdown region. Hence a regulated Dc output voltage $V_0 = V_Z$ is obtained across R_L , whenever the input voltage remains within a minimum and maximum voltage. Basically there are two type of regulations such as:

Line Regulation: In this type of regulation, series resistance and load resistance are fixed, only input voltage is changing. Output voltage remains the same as long as the input voltage is maintained above a minimum value. Percentage Line regulation= $\left(\frac{\Delta V_{OUT}}{\Delta V_{IN}}\right) \times 100\%$.


Load Regulation: In this type of regulation, input voltage is fixed and the load resistance is varying. Output volt remains same, as long as the load resistance is maintained above a minimum value. Percentage Load regulation= $\left(\frac{V_{NL}-V_{FL}}{V_{FL}}\right)$ 100%.


• Components required:

Zener diode, resistor, rheostat, voltmeter, ammeter, DC source.

Software used: Proteus.

• Circuit diagrams:

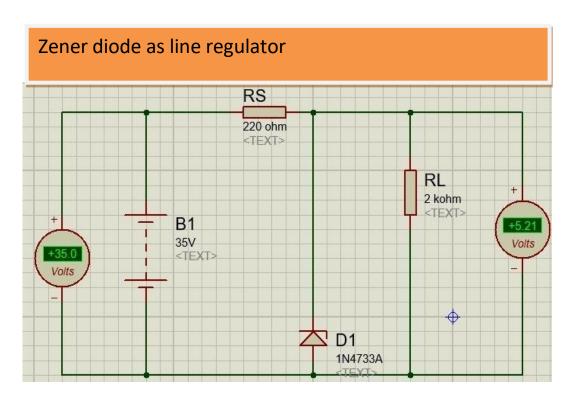

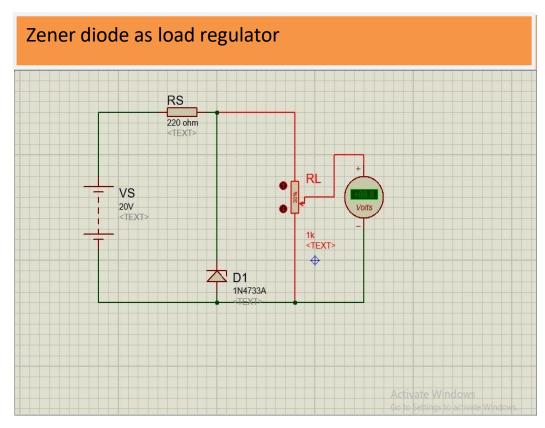

• Obervation Tables:

ZENER LINE REGULATION

Rs = 220 Ohm
Zener voltage (Vz) = 5.1 Volt
Rt = 2 Kohm

SL. NO.	UNREGULATED SUPPLY VOLTAGE (Vs) Volt	REGULATED OUTPUT VOLTAGE (Vo) Volt	% VOLTAGE REGULATION (Vo/Vs) x 100
1	1	0	50
2	2	1	50
3	3	1.5	50
4	4	2	50
5	5	2.5	50
6	6	3	50
7	7	3.5	50
8	8	4	50
9	9	4.5	50
10	10	4.94	49.4
11	11	5	45.45
12	12	5.03	41.92
13	13	5.04	38.76
14	14	5.05	36.07
15	16	5.07	31.68
16	18	5.09	28.28
17	20	5.1	25.5
18	25	5.1	20.4
19	30	5.1	17
20	35	5.2	14.85

Zener Load Regulation

Rs = 220 Ohm
Zener voltage (Vz) = 5.1 volt
Supply Voltage (Vs) = 20 Volt
No Load Voltage (VnL) = 5.14 Volt

SL. NO.	LOAD RESISTANCE (RL) Ohm	REGULATED OUTPUT VOLTAGE (VFL) Volt	% VOLTAGE REGULATION [(VNL - VFL)/VFL] x 100
1	1000	5.11	0.6
2	950	4.85	5.97
3	900	4.6	11.74
4	850	4.34	18.43
5	800	4.09	25.37
6	750	3.83	34.2
7	700	3.58	43.58
8	650	3.32	54.82
9	600	3.03	69.64
10	550	2.81	82.92
11	500	2.55	101.57
12	450	2.3	123.48
13	400	2.04	152
14	350	1.79	187.2
15	300	1.53	236

• Graphs:





• Precautions:

- 1. Make sure that the connections are tight.
- 2. Take care to apply suitable forward and reverse voltages across the zener diode so that suitable forward and reverse currents flow through the diode. Otherwise the diode may be damaged.

• Conclusion:

V-I reverse characteristics of Zener diode, we (Zener voltage, here R) the reverse voltage remains constant while the current goes on increasing abruptly. But, while performing the experiment it should be noted that the maximum current rating of the Zener is not cros operation. The forward characteristics of Zener are the same as that of a simple diode.

• References:

- ➤ https://www.electronics-tutorials.ws/diode/diode_7.html
- Electronics Fundamentals And Application D. Chattopadhyay & P.C. Rakshit (New Age International Publishers)

